

Correction Exercice 4

\o.v	00	01	11	10
0	0	0	0	0
1	1	1	1	1



$R = r$

\o.v	00	01	11	10
0	0	0	1	1
1	0	0	0	0

$O = r \cdot o$

\o.v	00	01	11	10
0	0	1	0	0
1	0	0	0	0

$V = r \cdot o \cdot v$

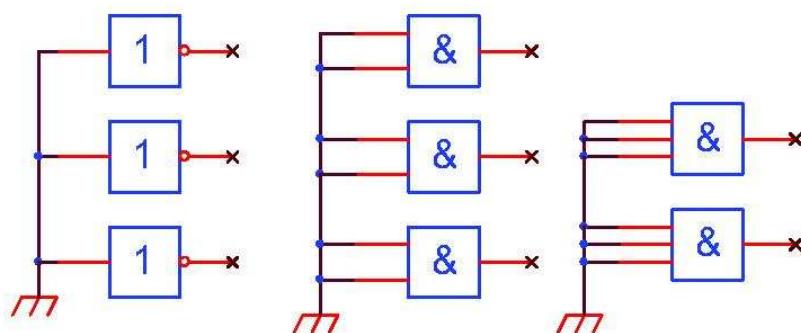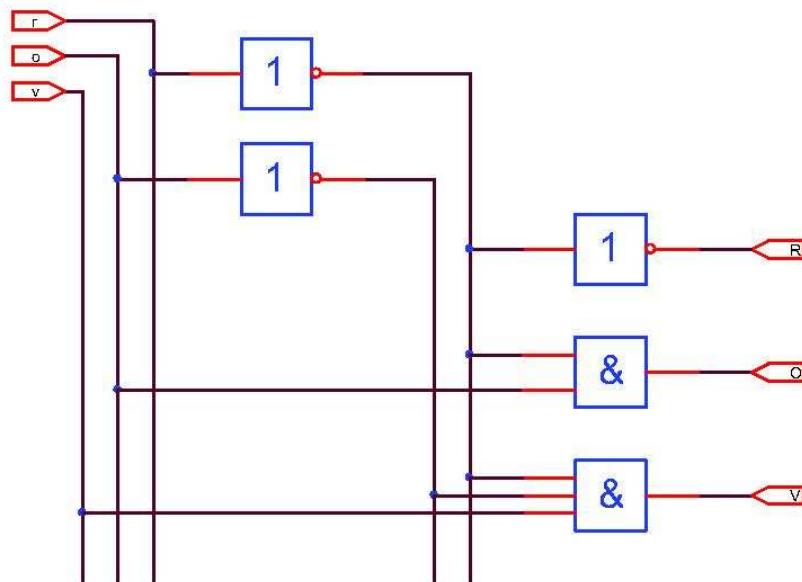

On utilise 3 Circuits intégrés.